

ANALOG CIRCUITS THEORY

ASSIGNMENT 1

Name: Rahul Mukundhan(IMT2022518)


mail: rahul.mukundhan@iiitb.ac.in

Section 1 – Theory

Analog Circuits - Assignment 2
IMT2022518 - Rahul M

Q1) V_{out} vs i_{in} , where diode has V_0 prob.

a)

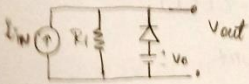

\Rightarrow let us assume that the case is reverse bias ($V_{out} - V_0 < 0$)
(V_0 shunt)

\leftarrow always: $\frac{V_{out} - V_0}{V_0 - V_0} = i_{in} R_1$

$\Rightarrow V_{out} = (i_{in}) R_1$

$= \frac{V_{out} - V_0}{V_0 - V_0} - 0$

\rightarrow Now, for forward bias:


$\frac{V_{out} - V_0}{V_0 - V_{out}} > V_0$, it conducts, so:
($V_0 + V_0 < V_{out}$)

$V_0 > V_{out} + V_0$


$\Rightarrow V_B - V_0 > (i_{in} R_1)$

$\frac{V_B - V_0}{R_1} > i_{in}$

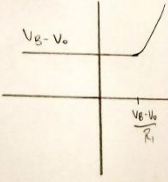$\Rightarrow f(i_{in}) = \begin{cases} V_B - V_0 / R_1 \text{ (inc.)} & \text{when } i \geq \frac{V_B - V_0}{R_1} \\ 0 & \text{otherwise} \end{cases}$



if $b >$

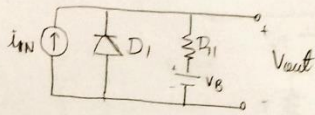

~~if forward bias exists.~~

use KVL:

$$i_{IN} R_1 + V_B + V_o = 0$$

$$i_{IN} = - \left(\frac{V_B + V_o}{R_1} \right)$$

\Rightarrow if D_1 is ON:

$$i_{IN} > - \left(\frac{V_B + V_o}{R_1} \right) \text{ s.t.}$$

$$V_B =$$


$$V_{out} = -V_o, \text{ then}$$



\Rightarrow if D_1 is OFF:

$$i_{IN} < - \left(\frac{V_B + V_o}{R_1} \right)$$

$$i_{IN} = - \frac{V_B}{R_1},$$


$$V_{out} = i_{IN} R_1 + V_B$$

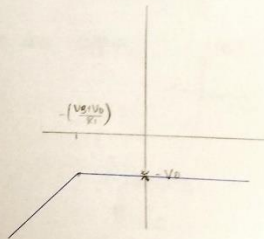

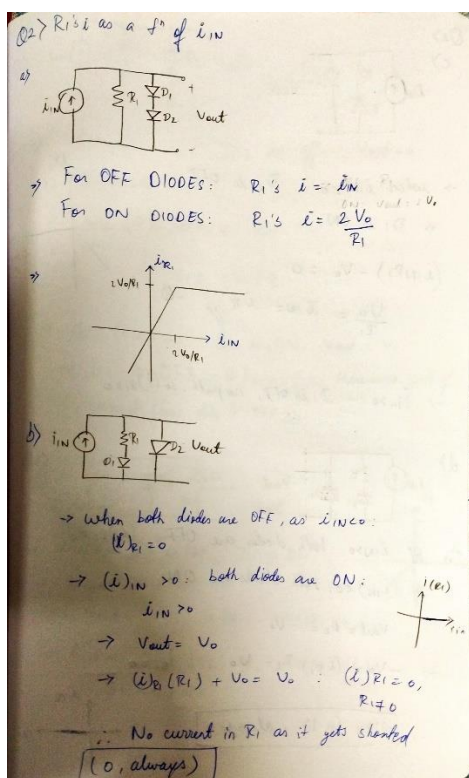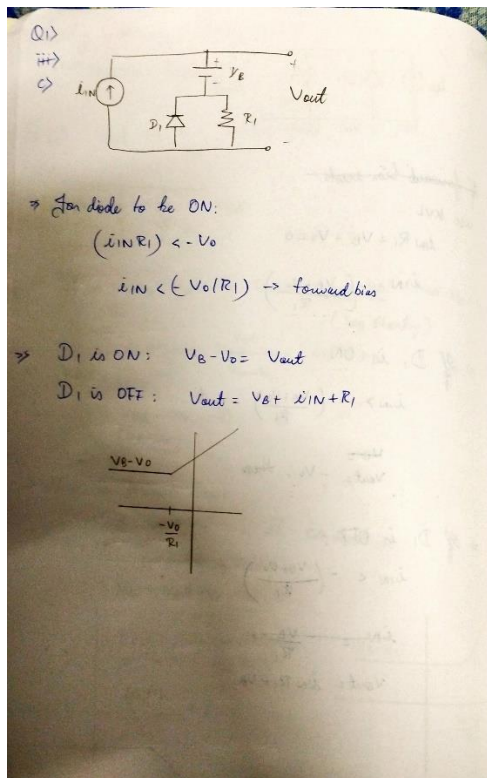

Q2>

c)

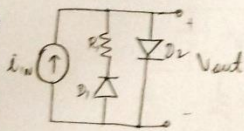


→ when $i_{in} < 0$: D_2 is OFF

→ D_1 is ON


$$(i_{in} R_1) - V_o = 0$$
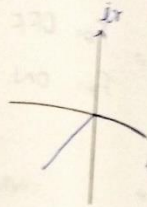
$$\frac{V_o}{R_1} = i_{in} = i_R \quad -0$$



→ $i_{in} > 0$: D_1 is OFF, no path, so $(i)_{R1} = 0$

d)

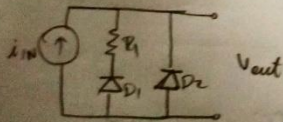


If $i_{in} > 0$: both diodes are OFF: $(i)_{R1} = 0$


If $(i_{in}) < 0$: both diodes are ON:

$$V_{out} = V_{D2} = -V_o$$

$$\Rightarrow -V_o = (i_{R1}) R_1 - V_o : i_{R1} = 0$$

∴ Like in b), always 0

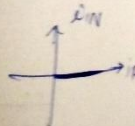

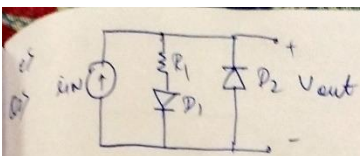

\Rightarrow when $(i_{in} > 0)$: D_2 is off: $V_{out} = 0$


$\Rightarrow D_1$ is ON

$$\Rightarrow i_{in} (i_{D1}) R_1 = V_0$$

$$(i)_{R1} = V_0 / R_1$$

\Rightarrow For $(i_{in} < 0)$: D_2 is ON, $V_{out} = V_0$

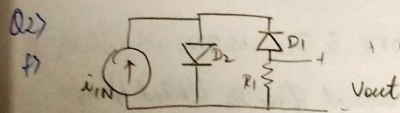$\Rightarrow D_1$ is OFF, $(i)_{R1} = 0$, as there is no path of current flow due to OFF D_1



$\Rightarrow i_{in} < 0$: D_2 is OFF, D_1 is ON


$$\rightarrow V_{out} + V_0 = 0$$

$$\rightarrow V_{out} = -V_0, (i)_{R1} = -V_0 / R_1 = i_{in}$$

$\Rightarrow i_{in} > 0$: D_1 is OFF, D_2 is ON, $(i)_{R1} = 0$, due to D_1 being OFF



Q2)

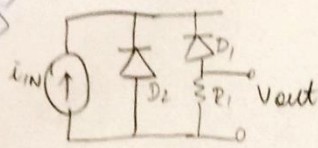


→ D_1, D_2 are OFF when $(i_{IN}) < 0$: $(i)_{R1} = 0$

→ D_1, D_2 are ON, when $(i_{IN}) > 0$:


$$V_{out} + V_D = V_0$$

$$\rightarrow V_{out} = V_0, (i_{R1})_{R1} = 0$$

$$(i)_{R1} = 0$$

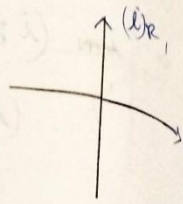

h)

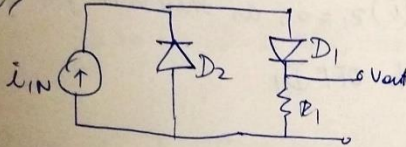

→ $(i_{IN}) < 0$: D_1 is OFF & D_2 is ON:

$(i)_{R1} = 0$, as current flow is blocked by D_1


→ $(i_{IN}) > 0$: D_2 is OFF, D_1 is ON:

$$\rightarrow V_{out} + V_D = 0$$


$$V_{out} = -V_0$$

$$\rightarrow (i_{R1})_{R1} = -V_0$$


$$(i)_{R1} = -V_0/R_1 = i_{IN}$$

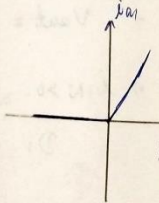

Q3) Full-wave Rectifier

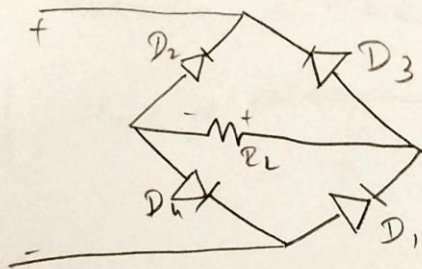

⇒ Problem: connection of D_3

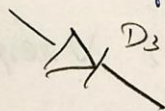


, but reversed here

⇒ During the positive half cycle, D_2 & D_3 will be reverse biased


⇒ $V_{out} = 0$, due to i in $R_L = 0$


⇒ During the negative half cycle, D_1 & D_3 are ON, short the input & once again, no current via R_L .

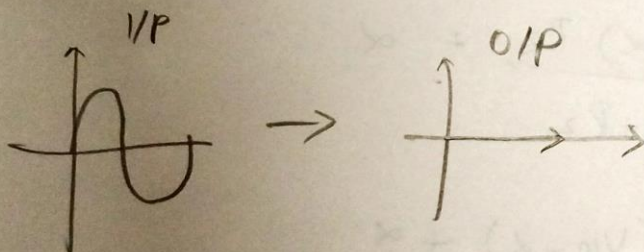⇒ No rectification, V_{out} is always $\boxed{0}$




Q4)

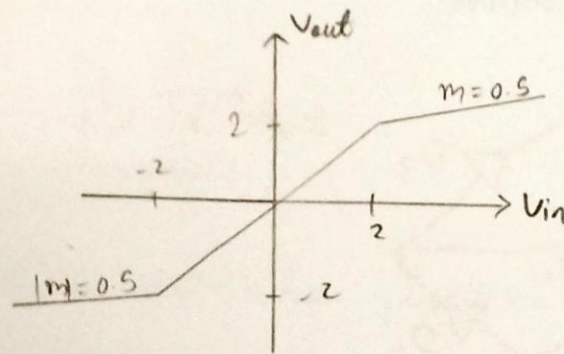

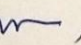Given: $1k\Omega$ , diodes ($V_0 = 0$), other components

\Rightarrow Take α, α' as 2, -2 V respectively, as:
 m goes from 1 to $1/2$

(m : slope)

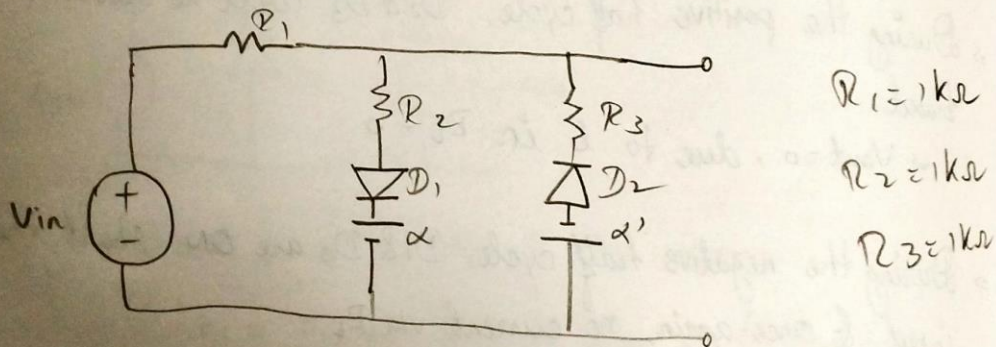

\Rightarrow If $V_{in} > \alpha$, D_2 is OFF
 D_1 is ON

$$V_{out} = \frac{(V_{in} - \alpha) R_2}{R_1 + R_2} + \alpha$$

$$= \frac{1}{2} (V_{in} - \alpha) + \alpha$$

$$= \frac{V_{in}}{2} + 1$$

Q4) $\alpha' < V_{in} < \alpha$: D_1 & D_2 are OFF

$\therefore V_{out} = V_{in}$, as $i = 0$

if $V_{in} < \alpha'$: D_1 is OFF
 D_2 is ON

$$V_{out} = -2 + \frac{(V_{in} + 1)R_3}{R_1 + R_3}$$

$$= -2 + \frac{(V_{in} + 2)R_3}{R_1 + R_3}$$


$$= -2 + 1/2 (V_{in} + 2)$$

$$= V_{in}/2 - 1$$

$< V_{in}/2$ comes when $R_1 = R_2 = R_3 = 1k\Omega$

Section 2- LTSPICE

Q5)

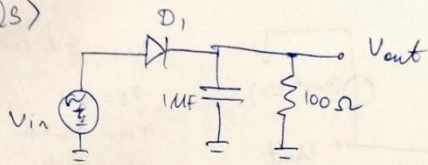

$V_{in}: 60\text{Hz}, 5\text{V}$

a) p-p ripple

$$\Rightarrow p-p = \frac{V_{in}}{fRC}, \quad f = 60\text{Hz}$$

$$R = 100\Omega$$

$$C = 1\mu\text{F}$$

$$= \frac{5}{10^{-6} \times 100 \times 60} = \frac{5}{6 \times 10^{-3}}$$

$$= \frac{5}{6} \times 1000 = \frac{5000}{6}$$


Q5)




a) p-p ripple: $V_r \approx 4.245191\text{V}$, so $V_p = 0\text{V}$

b) peak current

$$\rightarrow 42.48\text{mA}$$

(graphical observations)

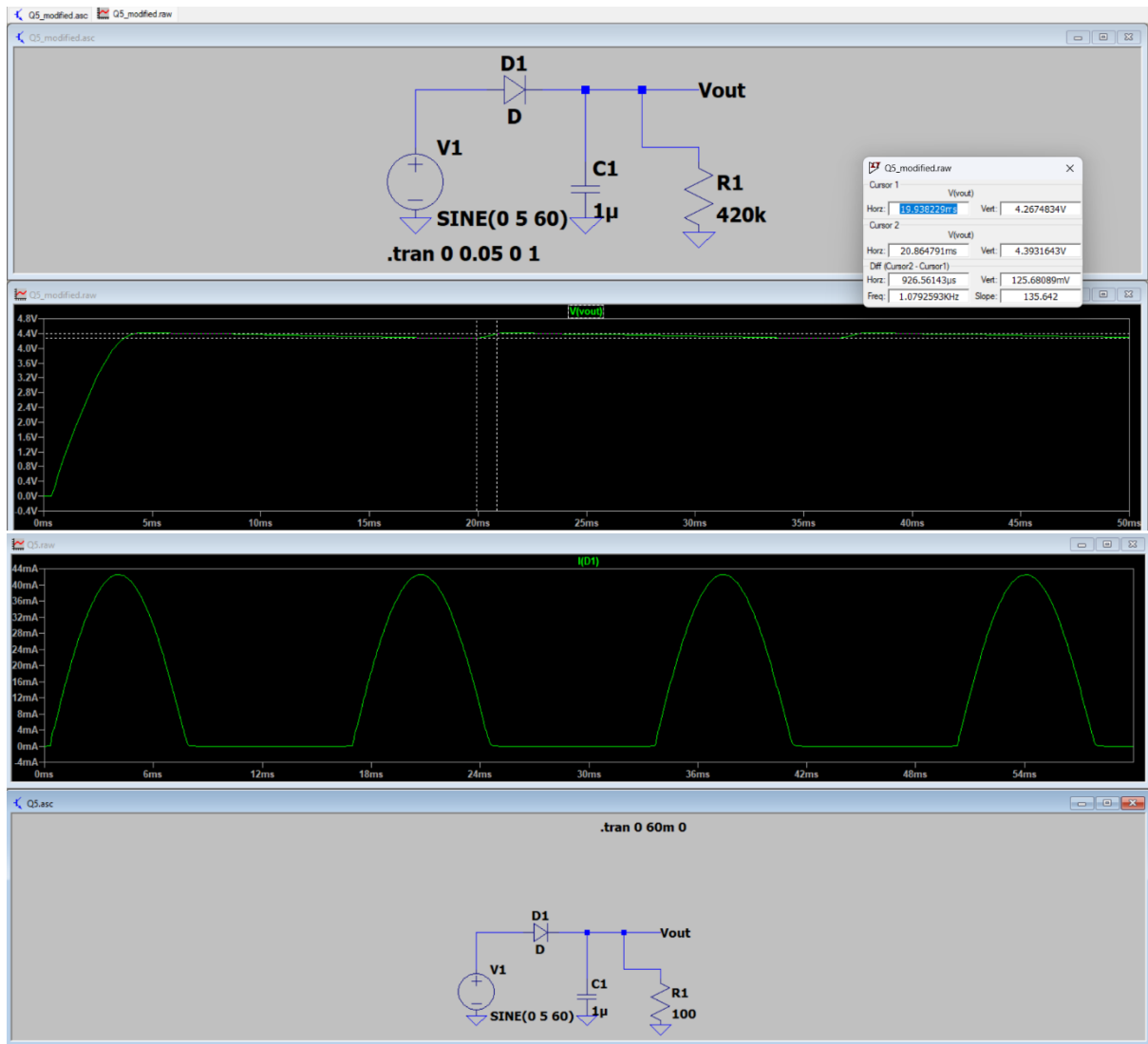

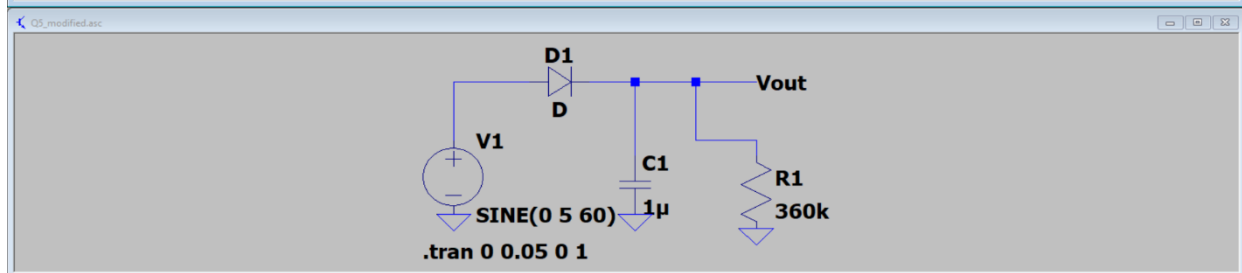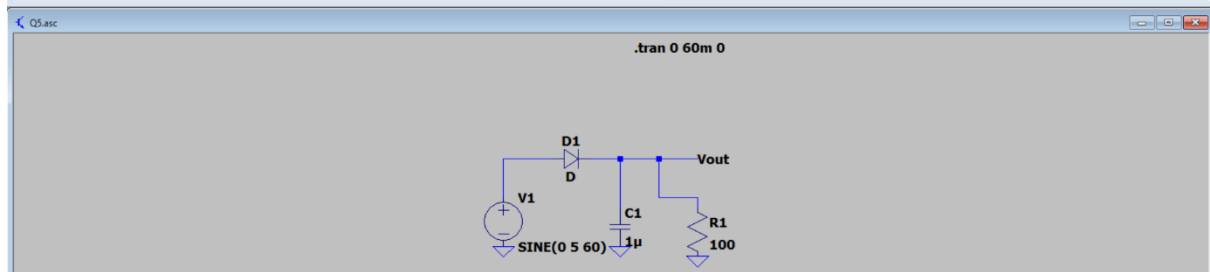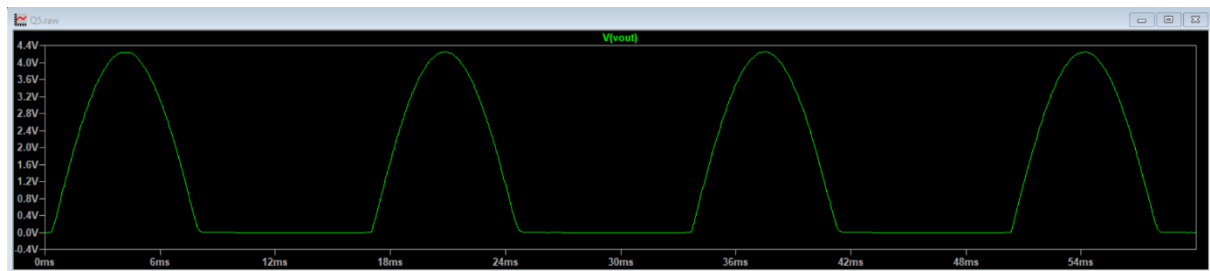

Q3)

c) \Rightarrow For this, let value of m be R

$$\rightarrow 200 \text{ mV} \geq \frac{V_p}{FRC} \quad (\text{here } V_0 = 0 \text{ V})$$

$$\rightarrow 0.2 \geq \frac{S}{60 \times R \times 10^{-6}}$$

$$\rightarrow R \geq \frac{S}{0.2 \times 60 \times 10^{-6}}$$

$$\rightarrow R \geq \frac{S \times 10^6 \times S}{60}$$

$$\rightarrow R \geq \frac{25}{60} \times 10^6$$

$$R \geq \frac{5}{12} \times 10^6$$

$$R \geq 416,666.67 \Omega$$

$$R \geq \approx 417 \text{ k}\Omega$$

$$\langle \text{Take } R = 420 \text{ k}\Omega \rangle$$


Q4) $V_0 = 0.76 \text{ V}, V_p = 4.24 \text{ V}.$

$$\rightarrow R \geq \frac{4.24}{0.2 \times 60 \times 10^{-6}}$$

$$R \geq 353,333 \Omega$$

$$R \approx 353 \text{ k}\Omega \quad (\geq)$$

Q6)

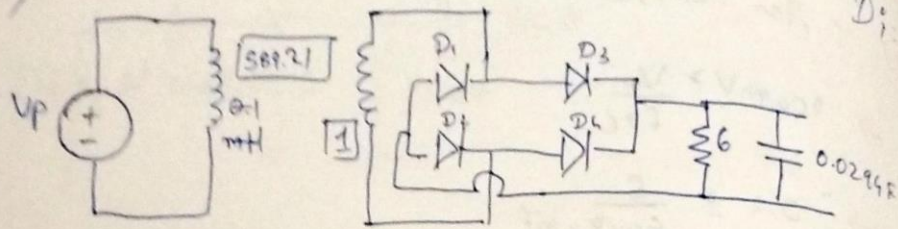

$$V_p = 230 \times \sqrt{2} \quad (V_{peak})$$

$$\rightarrow \frac{V_p}{13.4} = \frac{n_1}{n_2} \quad \left(@ \text{ o/p of } 13.4V, \text{ transformer should have } 12 + 0.2 \times 2 \right)$$

$$\rightarrow \frac{V_p}{13.4} = \frac{325.3}{13.4} = 24.22382$$

$$\therefore \frac{L_1}{L_2} \propto \left(\frac{n_1}{n_2} \right)^2$$

$$\therefore \frac{L_1}{L_2} = 589.21809 \rightarrow 589$$

$$\Rightarrow \frac{V_r}{V_p} = 0.05 \quad (\text{given})$$

\therefore DC component goes only in R , $\bar{i} = 2A$, $V = 12V$

$$\therefore R = 6\Omega$$

$$\rightarrow \frac{V_p - 2V_0}{2fRC} = \frac{1}{20}$$

$$\frac{(V_p) f R C}{V_p - 2V_0} = 10 \rightarrow \frac{(13.4)(50)(6)C}{12} = 10$$

$$\rightarrow C = 0.0294F$$

$$PIV: V_s - V_o$$

$$= 12.7V$$

$i_{avg} \rightarrow$

$$i_{max} = i_L \left(1 + 2\pi \sqrt{\frac{U_p}{2U_r}} \right)$$

$$= 2 \left(1 + 2\pi \sqrt{\frac{20}{2}} \right)$$

$$= 2 \left(1 + 2\pi \sqrt{10} \right)$$


$$i_{max} = 2 \left(1 + 2\pi \sqrt{10} \right)$$


$$\approx 41.74A$$

$i_{avg}:$

From graph, we can infer that
and $i_{avg} = 956.48mA$

$$PIV = 12.73V$$

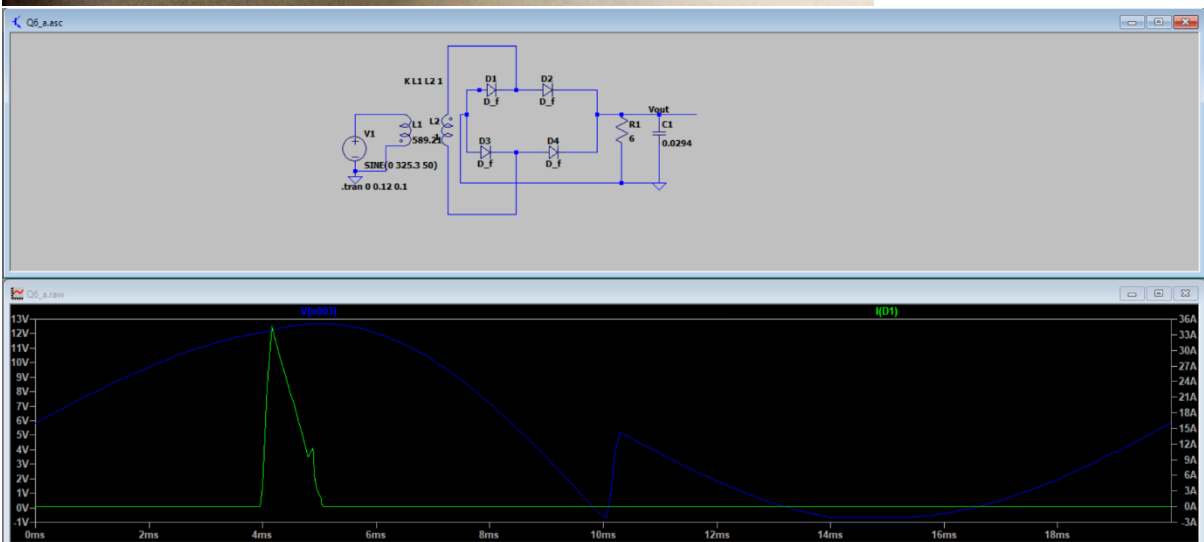

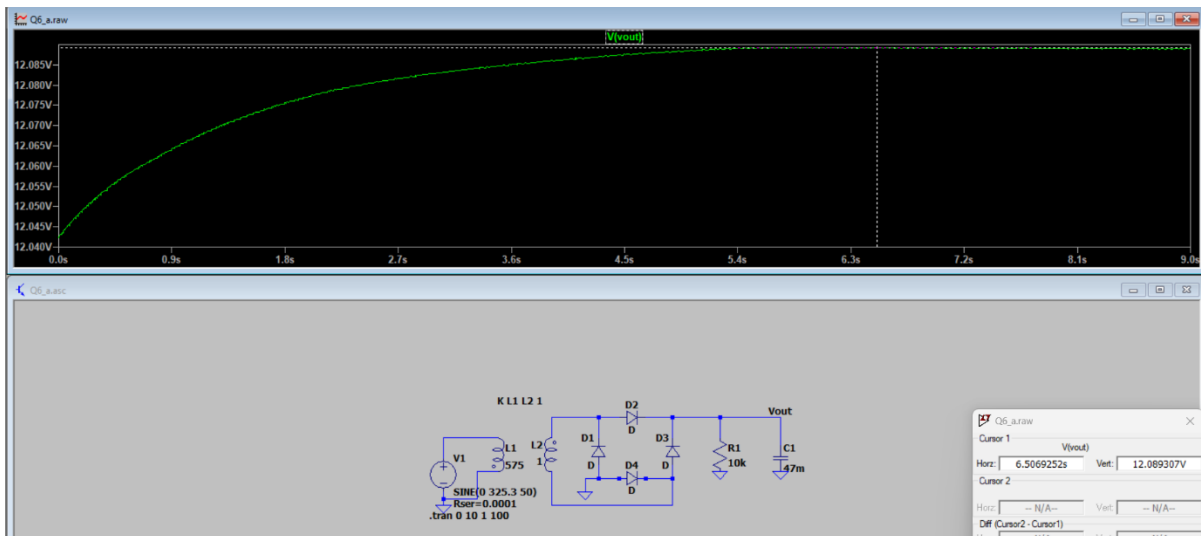

Q9a)

$V_{in} = 9V, 60Hz$
 $R_E = 50\Omega$
 $r_n = 5/2 k\Omega$
 $g_m = 0.1 S$

we know that

$$A_v = \frac{R_E (1 + g_m r_n)}{r_n + R_E (1 + g_m r_n)}, \quad V_{out} = (A_v) V_{in}$$

$$\Rightarrow 1 + g_m r_n = 1 + 0.1 \times 5/2 \times 10^3$$


$$= 1 + \frac{1}{10} \times \frac{25}{10} \times 10 \times 10 \times 10 = 251$$

$$A_v = \frac{50 (251)}{\frac{5}{2} \times 10^3 + 50 (251)} = \frac{50 (251)}{50 (251) + \frac{5 \times 10^3}{2} \times 100}$$


$$= \frac{50 (251)}{50 (251) + 25 \times 100}$$

$$A_v = \frac{50 (251)}{50 (251) + 25 \times 50 \times 2} = \frac{251}{251 + 25 \times 2} = \frac{251}{301}$$
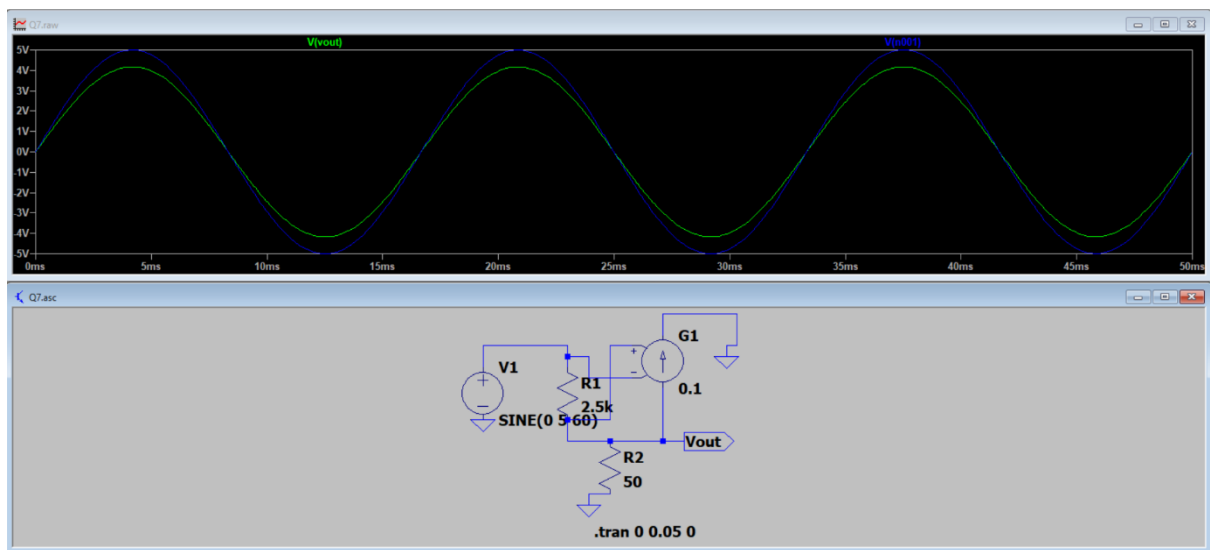
$$\Rightarrow V_{out} = \left(\frac{251}{301} \right) V_{in} \approx \frac{5}{6} \times 5 \approx \frac{25}{6} \rightarrow 4V \text{ approx.}$$



Q5)

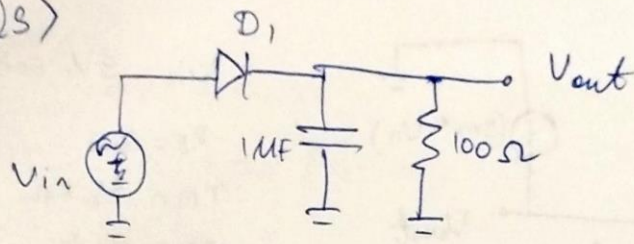

$V_{in}: 60 \text{ Hz}, 5 \text{ V}$

a) p-p ripple

$$\Rightarrow p-p = \frac{V_{in}}{fRC}, \quad f = 60 \text{ Hz}$$

$$R = 100 \Omega$$

$$C = 1 \mu\text{F}$$

$$= \frac{5}{10^{-6} \times 100 \times 60} = \frac{5}{6 \times 10^{-3}}$$

$$= \frac{5}{6} \times 1000 = \frac{5000}{6}$$

Q5)

a) p-p ripple: $V_r \approx 4.245191 \text{ V}$, so $V_p = 0 \text{ V}$

b) peak current

$$\rightarrow 42.48 \text{ mA}$$

(graphical observations)